
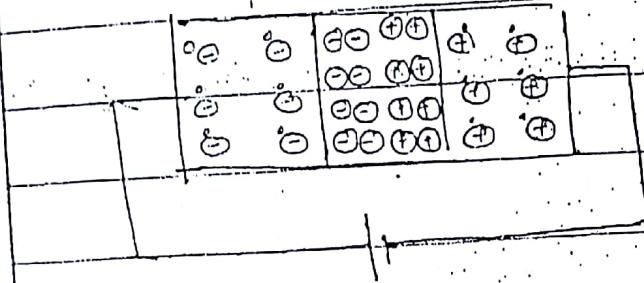
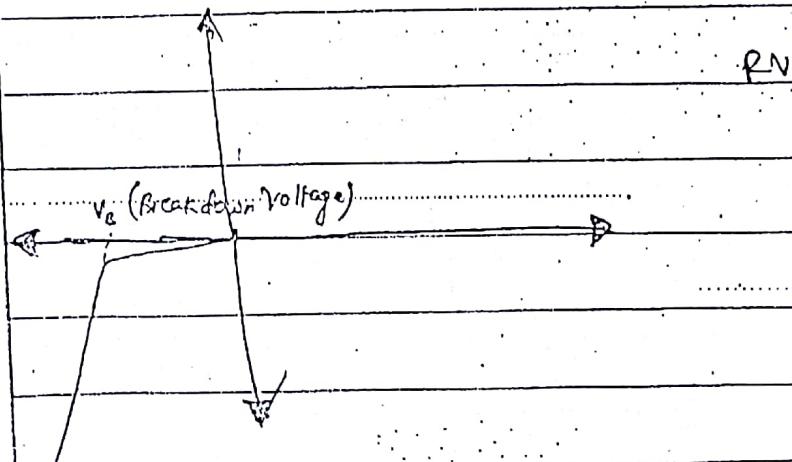



31 Oct 17

P - \longleftrightarrow N

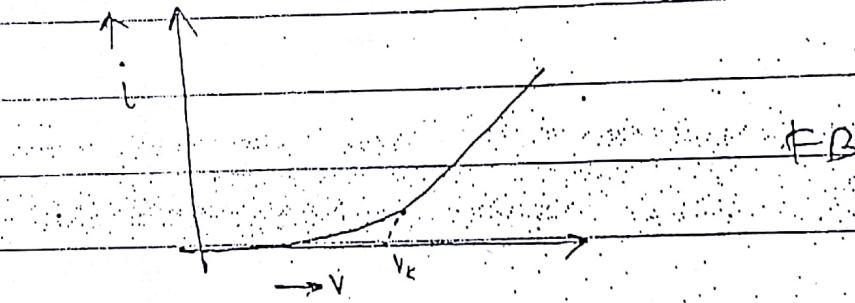PN junction can be set either as F.B (forward biased)
or Reverse Biased (RB)



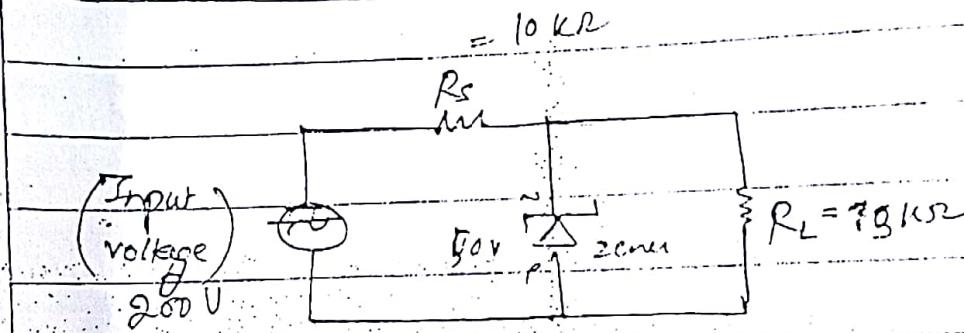- Date: _____
Page No. _____
- * Zener diode is a heavily doped p-n junction connected in reverse biased.
 - * It acts as a voltage stabilizer.
 - * It can be used across the load to maintain the constant voltage.
 - * In order to protect electronic device from voltage fluctuations.
 - * Zener diode is used



$$V = IR$$

$$I = \frac{V}{R} = \frac{200}{10 \times 10^3} = 20 \text{ mA}$$

if $I = \frac{100}{15 \times 10^3}$

$$I_L = \frac{100}{15 \times 10^3} = 10 \text{ mA}$$

$$I = I_L + I_Z$$

$$I_Z = 10 \text{ mA}$$

If voltage is 300V

$$I = \frac{300}{10 \times 10^3} = 30 \text{ mA}$$

Voltage Stabilisation Circuit :

* The Input voltage fluctuation would be observed by Series Resistor.

* Whereas Input current fluctuation are observed by Zener diode

As a result, the voltage acting across load and current flowing through a load remains constant. This is how Zener diode protects the load from Input Voltage fluctuations.


Bipolar Junction Transistors:

* BJT is a device prepared by using two p-n junctions.

It is basically used in oscillators and amplifiers.

* BJT are of two types : n-p-n & p-n-p

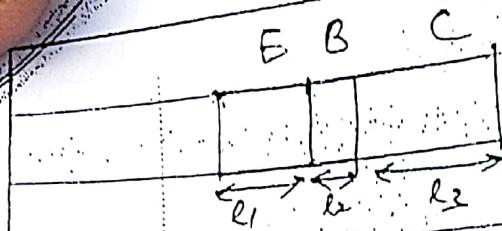* In BJT, we have three components : emitter, base, collector




$$\{ l_3 > l_1 > l_2 \}$$

- * emitter is doped heavily
- * base is doped very lightly
- * collector is doped moderately

- * In BJT - Emitter - Base junction is always connected in FB
Collector - Base junction is always connected in RB

- * Transistor means Transfer of resistance. A transistor can transmit current or can drive current from low resistance to high to. resistance terminal.

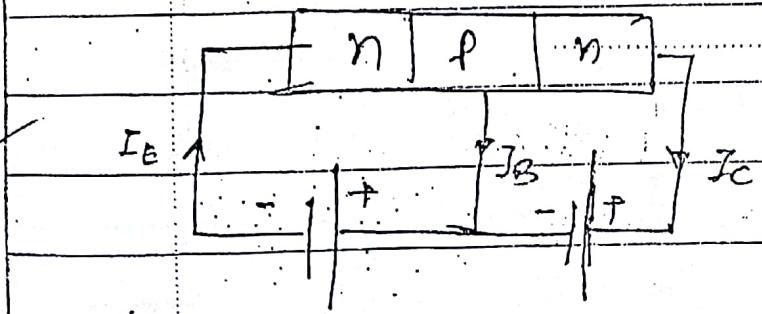- * As a result, signal @ voltage would be amplified




$$I_E = I_B + I_C$$


~~Voltage & power~~
BJT can be used as an amplifier.

2 Nov 17

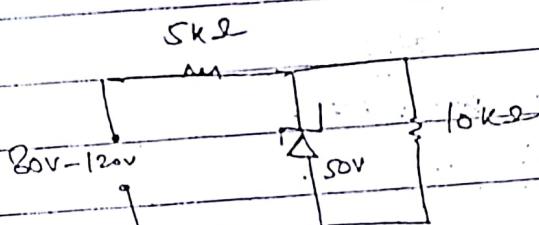Calculate min & max current that can pass through
Zener diode connected in the below diagram?


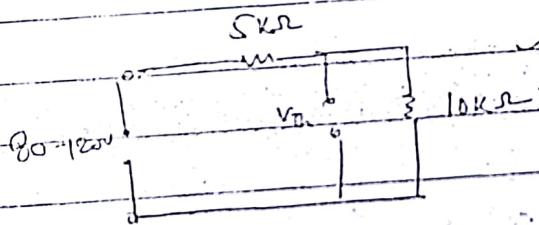
$$I_{\text{min}} = \frac{80 - 50}{5 \text{k}\Omega} = 6 \text{mA}$$



$$I_{\text{max}} = \frac{120 - 80}{5 \text{k}\Omega} = 14 \text{mA}$$

$$i = \frac{80}{15 \text{k}\Omega} = \frac{80 \times 10^{-3}}{15} \text{ A}$$

Check
yourself

$$i = 5.33 \text{ mA}$$

$$V_{\text{Th}} = i \times 5 \text{k}\Omega$$

$$\{ V_{\text{Th}} = 26.6 \text{ V}$$


$$180 - 8mA$$

Bun

$$15k\Omega$$

$$V_{Th} = 8 \times 5 = 40V$$

~~Common Base configuration~~

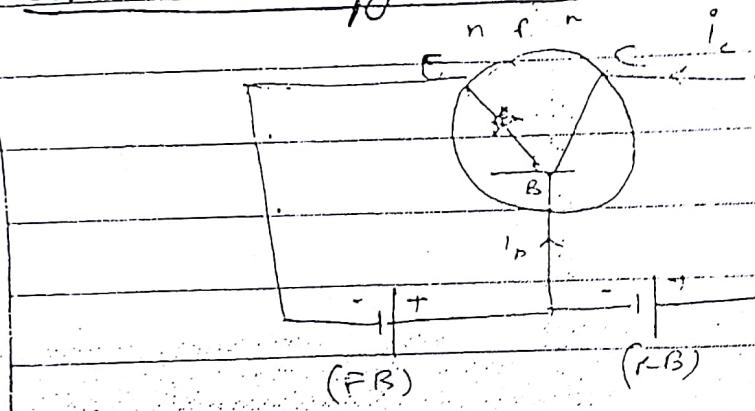

$$I_E = I_B + I_C$$

$$R_i = \frac{V_{BE}}{I_E}$$

$$R_o = \frac{V_{CE}}{I_C}$$

for Common Base configuration:
Current amplification factor:

$$\alpha = \frac{\Delta I_C}{\Delta I_E}$$


We know

$$\Delta I_C < \Delta I_E$$


$$\therefore \alpha < 1$$

usually, $\alpha \rightarrow 0.9$ to 0.998

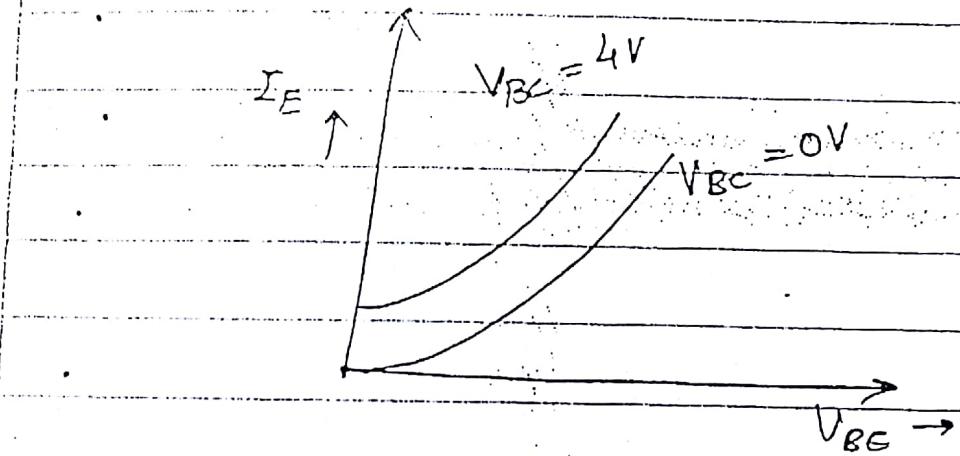* I/P characteristics in Common Base Configuration



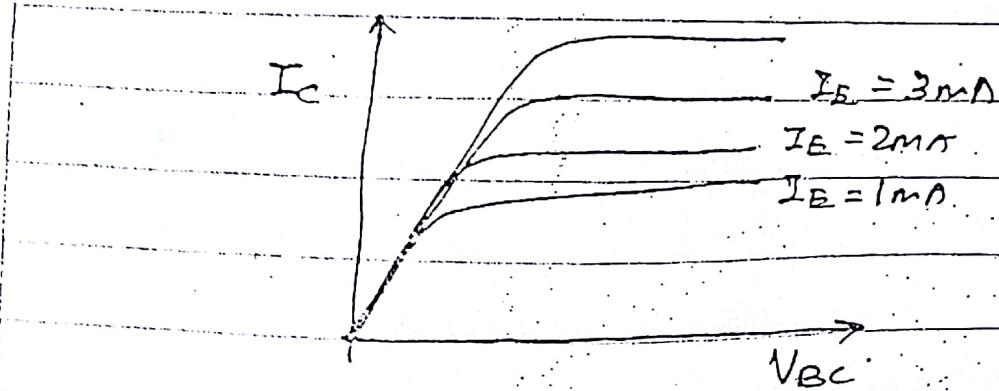* O/P characteristic Curve for Common Base Config.



* I_C Value is majority dependent on I_E and very little of V_{BC}

✓ (Needs correction)

Bunk Pages

A Common Base Transistor amplifier has an input resistance of $20\text{ k}\Omega$ and output resistance of $100\text{ k}\Omega$.
The collector load is $1\text{ k}\Omega$ if signal of 500 mV is applied b/w emitter and base. Then find the voltage amplification in this common base config. amplifier? (current amplification factor $\alpha \approx 1$)

$$R_i = 20\text{ k}\Omega$$

$$R_o = 100\text{ k}\Omega$$

$$V_{EBE} = 500\text{ mV}$$

~~$$R_o = 1\text{ k}\Omega$$~~

$$I_{BE} = \frac{500 \times 10^{-3}}{20} = 25\text{ mA}$$

$$I_{BC} \approx 25\text{ mA}$$

$$V_{BC} = I_{BC} \times 100\text{ k}\Omega$$


$$\approx 25\text{ mA} \times 100 \times 10^3$$

$$V_{BC} = \underline{2500\text{ V}} \quad 25 \times 10^3 \times 1000 \approx 25$$

$$\alpha = \frac{V_{BC}}{V_{BE}} = \frac{2500}{500 \times 10^3} = \frac{25000}{500 \times 10^3}$$

$$\alpha = \frac{500}{50} = 10$$

* Common-Emitter Configuration:

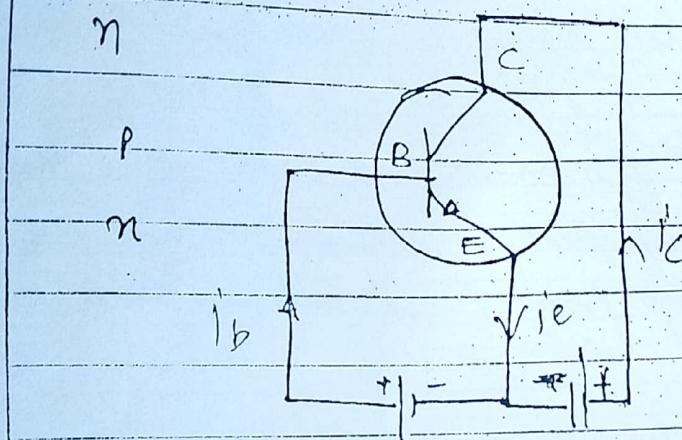

* In Common emitter Config, the current amplification factor is denoted by β

$$\beta = \frac{\Delta I_C}{\Delta I_B}$$

$$\beta > 1$$

Usually, $\beta \rightarrow 20$ to 500

~~✓~~ Reln b/w α & β :

$$\beta = \frac{\Delta I_C}{\Delta I_B}$$

$$\alpha = \frac{\Delta I_C}{\Delta I_E}$$

$$I_E = I_B + I_C$$

$$\Delta I_E = \Delta I_B + \Delta I_C$$

$$\Delta I_B = \Delta I_E - \Delta I_C$$

$$\beta = \frac{\Delta I_c}{\Delta I_E - \Delta I_c}$$


$$\beta = \frac{\Delta I_c}{\Delta I_E}$$

$$1 - \frac{\Delta I_c}{\Delta I_E}$$

$\boxed{\beta = \frac{\alpha}{1-\alpha}}$

3-Nov-7

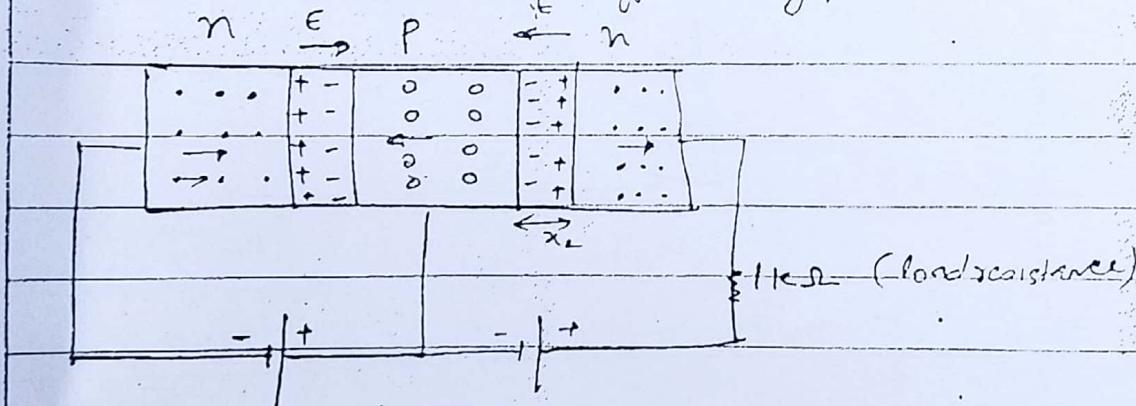~~Beta~~ R_{in} input resistance - resistance offered by p-n junction



* x_2 increases \Rightarrow Base width increases
Collector junction size increases

$$\frac{I = V}{ER} = \frac{500 \text{ mV}}{2 \text{ V}}$$

$$\alpha = \frac{\Delta I_c}{I_c}$$

$$I_{EC} = 25 \text{ mA}$$



E^- cannot face any resistance by Base-Collector junction because E^- is in opposite direction \Rightarrow attracting e^-

$$V_{BC} = I_{BC} R_L \\ = 25 \text{ mV} \times 10^3$$

$$V_{BC} = 25 \text{ V}$$

* Voltage amplification factor = $\frac{V_{BC}}{V_{BE}} = \frac{25}{500 \times 10^{-3}} = 50$

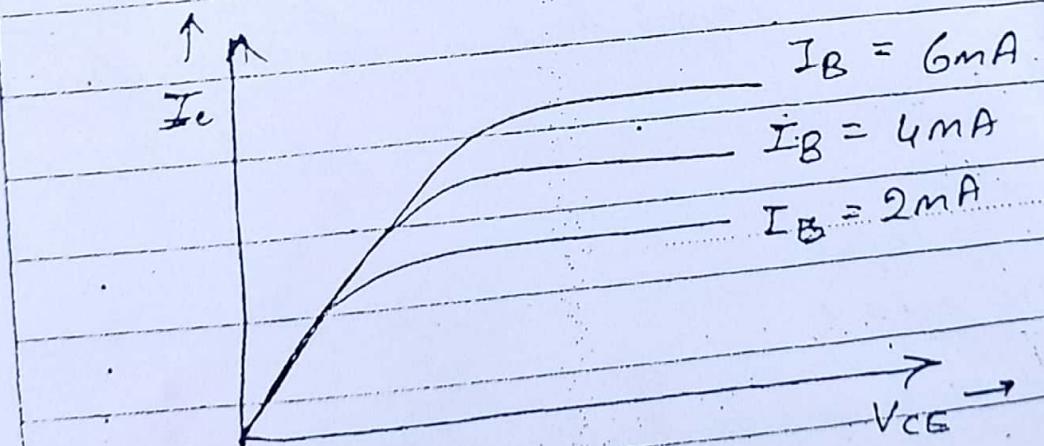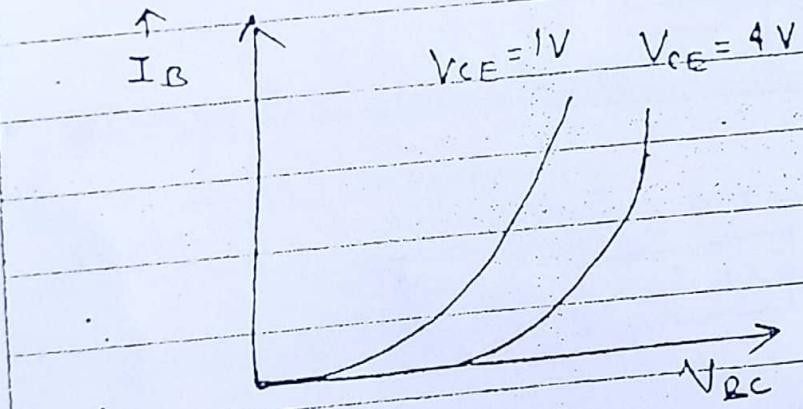~~emitter~~
Common collector configuration / characteristics:



* → BJT
→ FET

Bunk Pages

Field effect Transistors (FET) :

* Disadvantages of BJT :

- * BJT input impedance is low (BJT - low impedance)
- * Noise will be very high (High Noise)
↳ fluctuations produced in current, voltage & power?
- * Input impedances has its own effect (FET - high input impedance)
- # FET have high input impedance and low noise. (Low Noise)
- * BJT is a current controlled device. that is output current is controlled by input current ↳ BJT is current control device
- { FET is voltage controlled device?
↳ FET is voltage controlled device?
- # FET is a Voltage current device. That is O/P characteristics are controlled by voltage but not current.
- * In BJT we have n-p-n or p-n-p. (two type of charge carriers holes and electrons)
- # In FET, we have current is due to one type of charge carrier.

Types of FET:

MOSFET

(i) JFET

(Junction Field effect Transistor)

(i) n-channel JFET

(ii) p-channel JFET

Gate
(Control the e^-)

Source
(give the e^-)


Drain (Collect the e^-)

(n type slab)

(This n channel JFBT)

* Source - Gate is connected in
Reversed Biased.

* Working condition of FET:

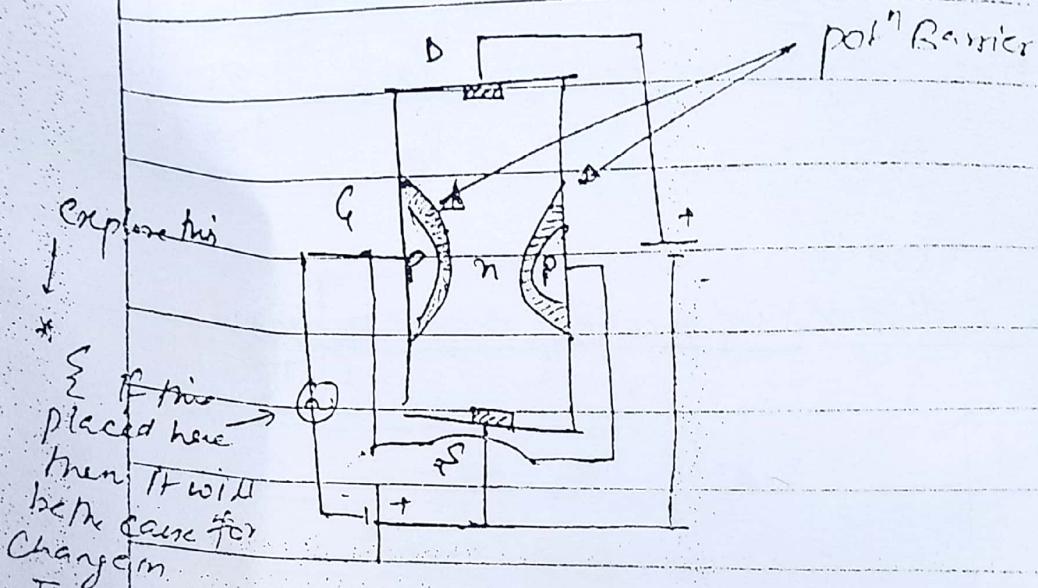

I_d = I_s Here, an important factor

$$I_d = I_s$$


* Once the potⁿ barrier increase touch each other, then
I_d = 0

* G-S is input

* S-D is output

* FET can be used as amplifiers (do yourself)


* Output characteristic curves:

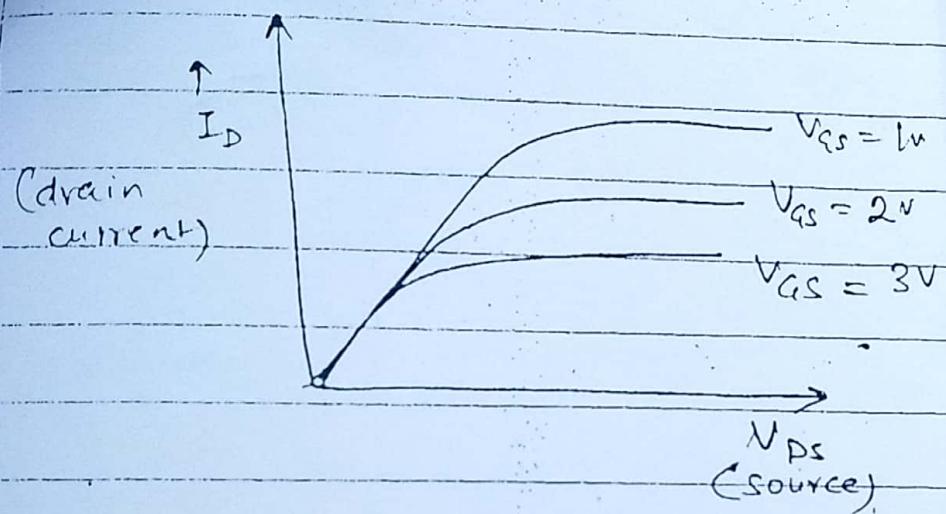

* Difference B/w BJT & FET:

- | BJT | FET |
|-------------------------------|--|
| * Two types of charge carrier | * There is only one type of charge carrier |
| * low input impedance | * high input impedance |
| * current controlled device | * voltage controlled device |
| * Noise is high | * Noise is less for FET |


Tunnel diode

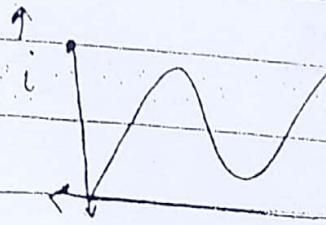

In earlier days,


people used to use this in oscillating circuits.

(forward Biased)

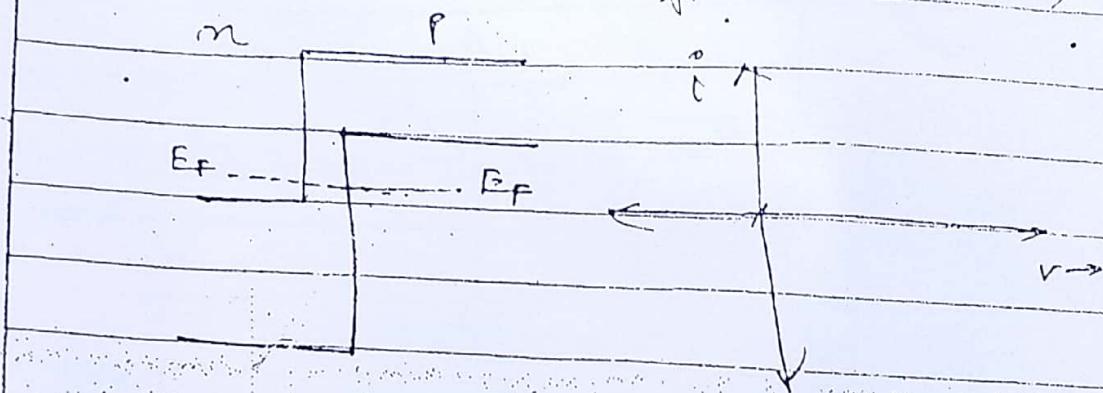

When forward bias is applied, then there is shift in Fermi energy level of the material (we are observing about new state in _____)

Empty Energy states

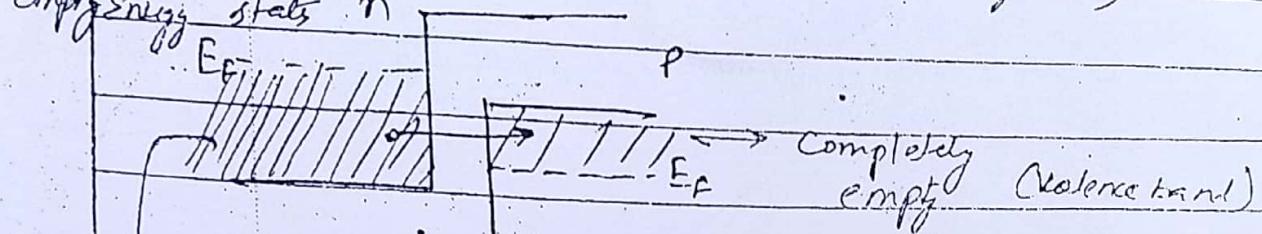

Completely
filled

Conduction band at 0°C

Completely filled Energy levels (at $-\infty$)

Bruno Rogers

E_P

E_F

i

V

E_P

E_F

i

V

Important topics :

* Postulates of free electron theory
Advantages and disadvantages

* Density of states function

* Fermi distribution function its significance
(It gives you occupancy of energy states by e^{-})

* Problems related to Fermi function

* Carrier concentration derivation

* Intrinsic carrier concentration derivation

* Intrinsic carrier concentration problem (most difficult)

* Complete understanding of intrinsic carrier concentration

* Application of Fermi distribution (Sheet notes)

* Problems on compensated semiconductors

Eg: Electrons and holes compensated in P-type semiconductor

* Hall effect

* Variation of Fermi level with Temp.

* Hall effect

* Gradient dependent absorption in Semiconductors

* Built-in polarization of a p-n junction

* Breakdown distribution of Fermi function (Breakdown, Penetration)

* Tunnel diode

* Laser diode

* LED (Light emitting diode)