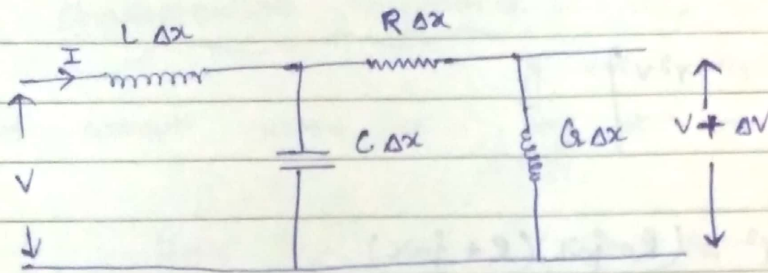


Transmission Lines

Transmission line acts as a communication media
e.g. 2 wire line, co-axial lines

- the communication b/w transmitter & receiver through a transmission line is called wire line communication.



Transmission Line

R - Resistance

L - Inductance

C - capacitance

G - admittance

Z - impedance

I - current

ΔV - voltage drop across arms

$$\Delta V = -(R\Delta x + j\omega L\Delta x)I$$

$$\Rightarrow \frac{\Delta V}{\Delta x} = -(R + j\omega L)I \quad \text{--- (1) ---} \quad \text{total impedance}$$

$$\text{at } x \rightarrow 0 \quad \boxed{\frac{dv}{dx} = -ZI} \quad \text{--- (A) ---} \quad \boxed{Z = R + j\omega L}$$

$$\text{Now,} \quad \Delta I = -(G\Delta x + j\omega C\Delta x)V$$

$$\frac{\Delta I}{\Delta x} = -(G + j\omega C)V$$

at $x \rightarrow 0$

$$\boxed{\frac{dI}{dx} = -YV} \quad \text{--- (2) ---} \quad \boxed{Y = \text{total admittance}}$$

Now, differentiating (a) w.r.t x

$$\frac{d^2V}{dx^2} = - (R + j\omega L) \frac{dI}{dx}$$

So,

$$\frac{d^2V}{dx^2} = + (R + j\omega L)(G + j\omega C)V$$

$$\left[\frac{d^2V}{dx^2} = \gamma^2 V \right]$$

where

$$\gamma^2 = (R + j\omega L)(G + j\omega C)$$

Similarly in z -dir.

$$\left[\frac{d^2V}{dz^2} = \gamma^2 V \right]$$

* All the eqn(s) are applicable to transient soln of both V and I and are fr of x or in general t.

* Soln of Transmission Line Equations :-

Soln of $\frac{d^2V}{dx^2} = \gamma^2 V$ is

$$V = V_+ e^{-\gamma x} + V_- e^{\gamma x} = V_+ e^{-\alpha x} e^{-j\beta x} + V_- e^{\alpha x} e^{j\beta x}$$

$$\left[\gamma = \alpha + j\beta \right]$$

where V_+ and V_- represent complex quantities.

$e^{-j\beta x} \rightarrow$ wave travelling in +ve x dir.

$e^{j\beta x} \rightarrow$ wave going in -ve x dir.

$\left[\beta x \rightarrow \text{electrical length of the line} \right]$

also,



$$I = Y_0 [V_+ e^{-\gamma x} - V_- e^{\gamma x}]$$

$$\Rightarrow Y_0 [V_+ e^{-\alpha x} e^{-j\beta x} - V_- e^{\alpha x} e^{j\beta x}]$$

Characteristic Impedance (Z_0) of line is defined as the ratio of +ve transmitting voltage to the line current wave at any pt. on line

$$Z_0 = \frac{V_+}{I_+} = \frac{V_-}{I_-}$$
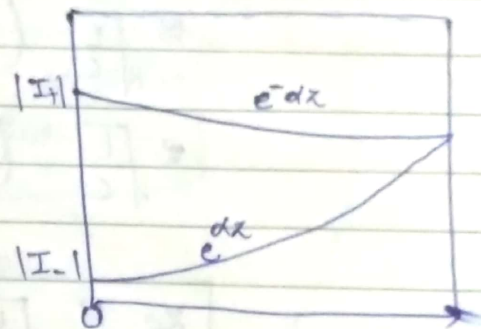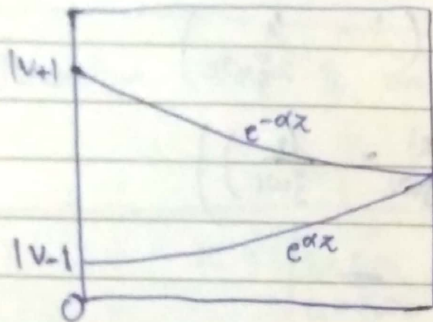
$$\text{and } Z = \frac{1}{Y_0} = \sqrt{\frac{Z}{Y}} = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$



At microwave frequencies it can be seen that $R \ll \omega L$ and $G \ll \omega C$

$$Y = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$\sqrt{(j\omega)^2 LC} \sqrt{\left(1 + \frac{R}{j\omega L}\right)\left(1 + \frac{G}{j\omega C}\right)}$$

$$\approx j\omega \sqrt{LC} \left[\left(1 + \frac{R}{2j\omega L}\right) \left(1 + \frac{G}{2j\omega C}\right) \right]$$

$$\approx j\omega \sqrt{LC} \left[1 + \frac{1}{2} \left(\frac{R}{j\omega L} + \frac{G}{j\omega C} \right) \right]$$

$$\gamma = \frac{1}{2} \left(R \sqrt{\frac{C}{L}} + G \sqrt{\frac{L}{C}} \right) + j\omega \sqrt{LC}$$

$$\gamma = \alpha + j\beta$$

$$\alpha = \frac{1}{2} \left(R \sqrt{\frac{C}{L}} + G \sqrt{\frac{L}{C}} \right)$$

$$\beta = \omega \sqrt{LC}$$

∴, the characteristic impedance is found to be

$$Z_0 = \sqrt{\frac{R + j\omega L}{R + j\omega C}}$$

$$\therefore \sqrt{\frac{L}{C}} \left(1 + \frac{R}{j\omega L} \right)^{1/2} \left(1 + \frac{G}{j\omega C} \right)^{1/2}$$

$$\approx \sqrt{\frac{L}{C}} \left(1 + \frac{R}{2j\omega L} \right) \left(1 - \frac{G}{2j\omega C} \right)$$

$$\approx \sqrt{\frac{L}{C}} \left(1 + \frac{1}{2} \left(\frac{R}{j\omega L} - \frac{G}{j\omega C} \right) \right)$$

$$\boxed{Z_0 \approx \sqrt{\frac{L}{C}}}$$

So, phase velocity

$$\left[u_p = \frac{\omega}{\beta} = \frac{1}{\sqrt{LC}} \right]$$

* Transmission lines can be characterized into 3 categories:-

- ① Loss less line
- ② Distortion less line
- ③ Low loss line

* Loss less line are one in which at radio frequency microwave frequency, the inductive reactance is much larger than that series resistance & capacitive reactance is much larger than shunt resistance.

$$R = G = 0$$

$$R \ll \omega L \quad \& \quad G \ll \omega C$$

* Distortion line is one in which condition $\frac{R}{L} = \frac{G}{C}$ is satisfied

$$Z = \frac{\sqrt{R + j\omega L}}{\sqrt{G + j\omega C}} = R_0 + jX_0$$

Using condⁿ of ~~loss~~ loss less line

$$Z = \frac{\sqrt{j\omega L}}{\sqrt{j\omega C}} \Rightarrow \sqrt{\frac{L}{C}}$$

$$\text{So, } R_0 = \sqrt{\frac{L}{C}}$$

$$\text{So, } R_0 = \sqrt{\frac{L}{C}} \quad \& \quad X_0 = 0$$

→ Characteristic Impedance of line is purely resistive

distortion less line:-

$$Z = \sqrt{\frac{R + j\omega L}{G + j\omega C}} = \sqrt{\frac{R}{G} \left(\frac{1 + R/j\omega L}{1 + G/j\omega C} \right)}$$

in distortion less line,

$$\frac{R}{L} = \frac{G}{C}$$

$$\frac{R}{G} = \frac{L}{C}$$

$$Z = \sqrt{\frac{L}{C} \left(\frac{1 + G/j\omega C}{1 + G/j\omega C} \right)}$$

$$Z = \sqrt{\frac{L}{C}}$$

$$R_0 = \sqrt{\frac{L}{C}} \neq X_0 = 0$$

* distortion less line are loss less line.

* low loss line:-

$$Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}} \Rightarrow \sqrt{\frac{j\omega L}{j\omega C} \left(\frac{1 + R/j\omega L}{1 + G/j\omega C} \right)}$$

$$Z_0 = \sqrt{\frac{L}{C}} \left(1 + \frac{R}{j\omega L} \right)^{1/2} \left(1 + \frac{G}{j\omega C} \right)^{-1/2}$$

$$Z_0 = \left(\frac{L}{C}\right)^{1/2} \left(1 + \frac{R}{2j\omega L}\right) \left(1 - \frac{G}{2j\omega C}\right)$$

$$\left(\frac{L}{C}\right)^{1/2} + \frac{1}{2}$$

$$\left(\frac{L}{C}\right)^{1/2} \left(1 + \frac{R}{2j\omega L} - \frac{G}{2j\omega C}\right)$$

$$\sqrt{\frac{L}{C}} + \frac{1}{2} \left[\frac{R}{j\omega} \left(\frac{L}{C}\right)^{1/2} \right] - \left[\frac{1}{2} \frac{G}{2j\omega C} \left(\frac{L}{C}\right)^{1/2} \right]$$

$$\sqrt{\frac{L}{C}} + \frac{1}{2j\omega} \left[\frac{R}{L} \sqrt{\frac{L}{C}} - \frac{G}{C} \sqrt{\frac{L}{C}} \right]$$

$$\boxed{R \approx \sqrt{\frac{L}{C}}}$$

$$X_0 = \frac{1}{2j\omega} \left(\frac{R}{\sqrt{LC}} - \frac{G\sqrt{L}}{C\sqrt{C}} \right)$$

* phase velocity :-

$$v_p = \omega/\beta$$

propagation constant

$$V(z) = V_+ e^{-\gamma z} + V_- e^{\gamma z}$$

$$I(z) = I_+ e^{-\gamma z} + I_- e^{\gamma z}$$

$\gamma \rightarrow$ ~~propo~~ propagation const.

$$\gamma = \alpha + j\beta$$

① loss less line

$$R = G = 0$$

$$\gamma = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$\gamma = j\omega \sqrt{LC} = \alpha + j\beta$$

$$\alpha = 0 \quad \beta = \omega \sqrt{LC}$$

$$\boxed{Z_p = \frac{1}{j\omega C}}$$

loss line has zero attenuation
constant $\alpha = 0$

② low loss line :-

$$R \ll \omega L \quad \& \quad G \ll \omega C$$

$$\gamma = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$\sqrt{(j\omega L)(j\omega C)} \sqrt{\left(1 + \frac{R}{j\omega L}\right)\left(1 + \frac{G}{j\omega C}\right)}$$

$$\gamma = j\omega \sqrt{LC} \left[1 + \frac{1}{2} \left(\frac{R}{j\omega L} + \frac{G}{j\omega C} \right) \right]$$

$$j\omega \sqrt{LC} + \frac{1}{2} \left[\frac{R \sqrt{C}}{\sqrt{L}} + \frac{G \sqrt{L}}{\sqrt{C}} \right]$$

$$j\omega \sqrt{LC} + \frac{1}{2} \left(\frac{R}{Z_0} + G Z_0 \right)$$

$$\alpha = \frac{R}{2Z_0} + \frac{G Z_0}{2}$$

$$\beta = \omega \sqrt{LC}$$

$$r = \sqrt{2Y} = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

$$\boxed{u_p = \frac{\omega}{\beta} = 1/\sqrt{LC}}$$

iii) distortion line :-

$$\frac{R}{L} = \frac{G}{C}$$

$$r = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$= \sqrt{(j\omega L)(j\omega C)} \sqrt{\left(1 + \frac{R}{j\omega L}\right)\left(1 + \frac{G}{j\omega C}\right)}$$

$$j\omega \sqrt{LC} \left(1 + \frac{G}{j\omega C}\right) \quad \left[\text{as } \frac{R}{L} = \frac{G}{C}\right]$$

$$j\omega \sqrt{LC} \left(\frac{j\omega C + G}{j\omega C}\right)$$


$$\cancel{\sqrt{LC}} \cancel{j\omega C} \cancel{j\omega C} + \frac{G \sqrt{LC}}{1} \rightarrow G \sqrt{\frac{C}{L}}$$

$$G \sqrt{\frac{C}{L}} + j\omega \sqrt{LC}$$

$$\boxed{\alpha = G \sqrt{\frac{C}{L}} \quad \& \quad \beta = \omega \sqrt{LC}}$$

* Reflection coefficient :-

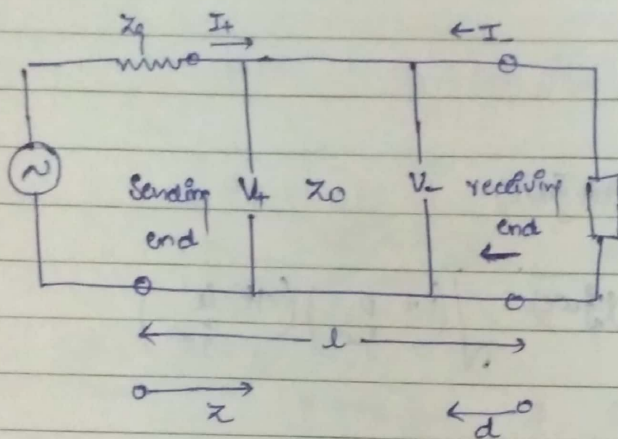Soln of transmission line contains 2 components: one travelling in the +ve z direction & the other travelling in the -ve z dir. If the load impedance is equal to the line characteristic impedance, reflected travelling wave does not exist.



Now,

$$V = V_+ e^{-\gamma z} + V_- e^{+\gamma z}$$

$$I = I_+ e^{-\gamma z} + I_- e^{+\gamma z}$$

Now, current can be expressed in terms of voltage

$$I = \frac{V_+}{Z_0} e^{-\gamma z} - \frac{V_-}{Z_0} e^{+\gamma z}$$

If the line has length l , then

$$V_l = V_+ e^{-\gamma l} + V_- e^{+\gamma l}$$

$$I_l = \frac{V_+}{Z_0} e^{-\gamma l} - \frac{V_-}{Z_0} e^{+\gamma l}$$

\Rightarrow Ratio of the voltage to the current at the receiving end is the load impedance Z_L .

$$Z_L = \frac{V_l}{I_l} = Z_0 \frac{V_+ e^{-\gamma l} + V_- e^{+\gamma l}}{V_+ e^{-\gamma l} - V_- e^{+\gamma l}}$$

Now,

Reflection coefficient, Γ (gamma) is defined as

$$\Gamma = \frac{\text{reflected voltage or current}}{\text{incident voltage or current}}$$

$$\left[\Gamma \equiv \frac{V_{ref}}{V_{inc}} = \frac{I_{ref}}{I_{inc}} \right]$$

$$\Gamma = \frac{V_- e^{-\gamma l}}{V_+ e^{-\gamma l}} = \frac{Z_L - Z_0}{Z_L + Z_0}$$

usually, it is a complex quantity.
So,

$$\Gamma_L = |\Gamma_L| e^{j\theta_L}$$

→ magnitude & never greater than unity
 $\theta \rightarrow$ phase angle b/w incident & reflected voltages at the receiving end

general soln is

$$\text{Ans a} \quad \Gamma = \frac{V_- e^{-\gamma z}}{V_+ e^{\gamma z}}$$

$$\Gamma = \frac{V_- e^{\gamma l}}{V_+ e^{-\gamma l}} \Rightarrow \frac{V_-}{V_+} e^{2\gamma l}$$

$$Z_L = \frac{V_L}{I_L} = Z_0 \left(\frac{V_+ e^{-\gamma l} + V_- e^{\gamma l}}{V_+ e^{-\gamma l} - V_- e^{\gamma l}} \right)$$

$$Z_L = Z_0 \frac{V_+ e^{-\gamma L}}{V_- e^{\gamma L}} \begin{pmatrix} 1 + \frac{V_- e^{\gamma L}}{V_+ e^{-\gamma L}} \\ 1 - \frac{V_- e^{\gamma L}}{V_+ e^{-\gamma L}} \end{pmatrix}$$

$$Z_L = Z_0 \begin{pmatrix} 1 + \Gamma_L \\ 1 - \Gamma_L \end{pmatrix}$$

$$Z_L (1 - \Gamma_L) = Z_0 (1 + \Gamma_L)$$

$$Z_L - \Gamma_L Z_L = Z_0 + \Gamma_L Z_0$$

$$Z_L - Z_0 = \Gamma_L (Z_L + Z_0)$$

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$